

ES Exam → 2012

DO NOT OPEN THIS TEST BOOKLET UNTIL YOU ARE ASKED TO DO SO

T.B.C. : R-FTF-M-FUA

Test Booklet Series

Serial No.

**A**

TEST BOOKLET  
ELECTRONICS AND  
TELECOMMUNICATION ENGINEERING  
( OBJECTIVE-TYPE )

PAPER—I

Time Allowed : Two Hours

Maximum Marks : 200

INSTRUCTIONS

1. IMMEDIATELY AFTER THE COMMENCEMENT OF THE EXAMINATION, YOU SHOULD CHECK THAT THIS TEST BOOKLET *DOES NOT* HAVE ANY UNPRINTED OR TORN OR MISSING PAGES OR ITEMS, ETC. IF SO, GET IT REPLACED BY A COMPLETE TEST BOOKLET.
2. ENCODE CLEARLY THE TEST BOOKLET SERIES A, B, C OR D AS THE CASE MAY BE IN THE APPROPRIATE PLACE IN THE ANSWER SHEET.
3. You have to enter your Roll Number on the Test Booklet in the Box provided alongside. *DO NOT* write *anything else* on the Test Booklet.
4. This Test Booklet contains **120** items (questions). Each item comprises four responses (answers). You will select the response which you want to mark on the Answer Sheet. In case you feel that there is more than one correct response, mark the response which you consider the best. In any case, choose *ONLY ONE* response for each item.
5. You have to mark all your responses *ONLY* on the separate Answer Sheet provided. See directions in the Answer Sheet.
6. All items carry equal marks.
7. Before you proceed to mark in the Answer Sheet the response to various items in the Test Booklet, you have to fill in some particulars in the Answer Sheet as per instructions sent to you with your Admission Certificate.
8. After you have completed filling in all your responses on the Answer Sheet and the examination has concluded, you should hand over to the Invigilator *ONLY* the *Answer Sheet*. You are permitted to take away with you the Test Booklet.
9. Sheets for rough work are appended in the Test Booklet at the end.
10. **Penalty for wrong answers :**  
THERE WILL BE PENALTY FOR WRONG ANSWERS MARKED BY A CANDIDATE IN THE OBJECTIVE TYPE QUESTION PAPERS.
  - (i) There are four alternatives for the answer to every question. For each question for which a wrong answer has been given by the candidate, **one-third (0.33)** of the marks assigned to that question will be deducted as penalty.
  - (ii) If a candidate gives more than one answer, it will be treated as a **wrong answer** even if one of the given answers happens to be correct and there will be same penalty as above to that question.
  - (iii) If a question is left blank, i.e., no answer is given by the candidate, there will be **no penalty** for that question.

DO NOT OPEN THIS TEST BOOKLET UNTIL YOU ARE ASKED TO DO SO

1. Match List-I with List-II and select the correct answer using the code given below the Lists :

<i>List-I</i>	<i>List-II</i>
A. Electrostriction	1. Converse of Seebeck effect
B. Ionic conductivity	2. Reverse effect of piezoelectricity
C. Peltier heat	3. Converse effect of magnetostriction
D. Villari effect	4. Conductivity of insulators

Code :

(a) A B C D  
2 4 1 3

(b) A B C D  
3 4 1 2

(c) A B C D  
2 1 4 3

(d) A B C D  
3 1 4 2

2. A piece of writing paper that is 10 cm wide, 15 cm long and 0.05 mm thick has a dielectric strength of 8 kV/mm. If it is placed between two copper plates and subjected to an increasing voltage, it will break down at

- (a) 8 kV  
(b) 4 kV  
(c) 0.4 kV  
(d) 0.8 kV

3. The concentration of hole-electron pairs in pure silicon at  $T = 300$  K is  $7 \times 10^{15}$  per cubic metre. Antimony is doped into silicon in a proportion of 1 atom in  $10^7$  atoms. Assuming that half of the impurity atoms contribute electrons in the conduction band, the factor by which the number of charge carriers increases due to doping (the number of silicon atoms per cubic metre is  $5 \times 10^{28}$ ) is

- (a)  $14 \times 10^{15}$   
(b)  $0.5 \times 10^{21}$   
(c)  $2.5 \times 10^{21}$   
(d)  $1.8 \times 10^5$

4. A potential barrier of 0.50 V exists across a  $p$ - $n$  junction. If the depletion region is  $5.0 \times 10^{-7}$  m wide, what is the intensity of the electric field in this region?

- (a)  $1.0 \times 10^6$  V/m  
(b)  $2.5 \times 10^{-7}$  V/m  
(c)  $2.5 \times 10^7$  V/m  
(d)  $2.5 \times 10^8$  V/m

5. In a transconductance, the device output

- (a) voltage depends upon the input voltage  
(b) voltage depends upon the input current  
(c) current depends upon the input voltage  
(d) current depends upon the input current

6. A flux of 1.2 mWb exerts in a magnet having a cross-section of  $30 \text{ cm}^2$ . The flux density in tesla is

- (a) 4
- (b) 0.4
- (c) 2.5
- (d) 40

7. If the drift velocity of holes under a field gradient of 200 V/m is 100 m/s, their mobility in SI units is

- (a) 0.5
- (b) 0.05
- (c) 50
- (d) 500

8. A bar magnet made of steel has a magnetic moment of  $2.5 \text{ A}\cdot\text{m}^2$  and a mass of  $6.6 \times 10^3 \text{ kg}$ . If the density of steel is  $7.9 \times 10^3 \text{ kg/m}^3$ , the intensity of magnetization is

- (a)  $8.3 \times 10^{-7} \text{ A/m}$
- (b)  $3 \times 10^6 \text{ A/m}$
- (c)  $6.3 \times 10^{-7} \text{ A/m}$
- (d)  $8.2 \times 10^6 \text{ A/m}$


9. An ideal low-pass filter has a cut-off frequency of 100 Hz. If the input to the filter in volts is  $v(t) = 30\sqrt{2} \sin 1256t$ , the magnitude of the output of the filter will be

- (a) 0 V
- (b) 20 V
- (c) 100 V
- (d) 200 V

10. Superconductors are becoming popular for their use in

- (a) generating very strong magnetic field
- (b) manufacture of bubble memories
- (c) generating electrostatic field
- (d) generating regions free from magnetic field

11.

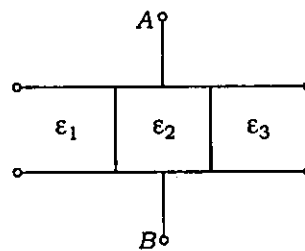

The space between the plates of a parallel-plate capacitor of capacitance  $C$  is filled with three dielectric slabs of identical size as shown in the figure. If dielectric constants are  $\epsilon_1$ ,  $\epsilon_2$  and  $\epsilon_3$ , the new capacitance is

- (a)  $\frac{C}{3}$
- (b)  $\frac{(\epsilon_1 + \epsilon_2 + \epsilon_3)C}{3}$
- (c)  $(\epsilon_1 + \epsilon_2 + \epsilon_3)C$
- (d)  $\frac{9(\epsilon_1 + \epsilon_2 + \epsilon_3)}{\epsilon_1 \epsilon_2 \epsilon_3}$

12. A capacitor of capacitance  $C$  is charged by connecting it to a battery of e.m.f.  $E$ . The capacitor is now disconnected and reconnected to the battery with the polarity reversed. The heat developed in the connecting wires is


(a)  $0.5CE^2$

(b)  $CE^2$

(c)  $2CE^2$

(d)  $3CE^2$

13.

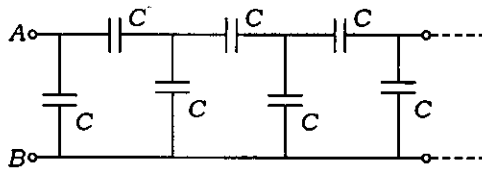

The effective capacitance across  $AB$  of the infinite ladder shown in the above figure is

(a)  $(1 + \sqrt{3})C$

(b)  $(1 + \sqrt{7})C$

(c)  $(1 + \sqrt{5})C$

(d)  $\frac{(1 + \sqrt{5})}{2}C$

14. Non-polar electrolytic capacitors

(a) are used for applications in AC circuits without any DC polarizing voltage

(b) contain two capacitors connected in series with opposing polarities

(c) Both (a) and (b) are correct

(d) Both (a) and (b) are wrong

15. Given

$N(E)$  : Density of states

$f(E)$  : Probability that a quantum state with energy  $E$  is occupied by an electron

$E_c$  : Energy level of conduction band

The expression  $\int_{E_c}^{\infty} N(E)f(E) dE$  gives

(a) minimum number of electrons in conduction band

(b) concentration of electrons in conduction band

(c) energy of electron concentration in conduction band

(d) conductivity of electrons in conduction band

16. Hall effect is useful for the measurement of a semiconductor's

- (a) mobility, carrier concentration and temperature
- (b) type (*n*-type or *p*-type), conductivity and temperature
- (c) type (*n*-type or *p*-type), mobility and carrier concentration
- (d) mobility, conductivity and temperature

17. The following equation describes a linear time-varying discrete time system

- (a)  $y(k+2) + ky(k+1) + y(k) = u(k)$
- (b)  $y(k+2) + ky^2(k+1) + y(k) = u(k)$
- (c)  $y(k+2) + 3y(k+1) + 2y(k) = u(k)$
- (d)  $y(k+2) + y^2(k+1) + ky(k) = u(k)$

18. A freewheeling diode in a phase-controlled rectifier

- (a) improves the line power factor
- (b) is responsible for additional reactive power
- (c) prevents inverse operation
- (d) is responsible for additional harmonics

19. The relative values of the forward conduction voltage for a *p-n* junction diode, a Red LED and a Schottky barrier diode are

- (a) Schottky voltage drop > *p-n* junction diode drop > Red LED drop
- (b) Red LED drop > *p-n* junction diode drop > Schottky voltage drop
- (c) *p-n* junction diode drop > Schottky voltage drop > Red LED drop
- (d) Schottky voltage drop > Red LED drop > *p-n* junction diode drop

20. Diodes are used to compensate which of the following transistor circuit parameters?

- 1.  $I_{CO}$
- 2.  $V_{BE}$
- 3.  $\beta$

- (a) 1 and 2 only
- (b) 2 and 3 only
- (c) 1 and 3 only
- (d) 1, 2 and 3

21. The  $I$ - $V$  characteristics of a tunnel diode exhibit

- (a) current-controlled negative resistance
- (b) voltage-controlled negative resistance
- (c) temperature-controlled positive resistance
- (d) current-controlled positive resistance

22. A gate to drain-connected enhancement mode MOSFET is an example of

- (a) an active load
- (b) a switching device
- (c) a three-terminal device
- (d) a diode

23. Thermal runaway is not possible in FET because, as the temperature of FET increases

- (a) the drain current increases
- (b) the mobility increases
- (c) the mobility decreases
- (d) the transconductance increases

24. The output impedance of a BJT under common-collector configuration is

- (a) low
- (b) high
- (c) medium
- (d) very high

25. Consider the following statements related to JFET :

1. Its operation depends on the flow of minority carriers only.
2. It is less noisy than BJT.
3. It has poor thermal stability.
4. It is relatively immune to radiation.

The correct statements are

- (a) 1, 2, 3 and 4
- (b) 1 and 2 only
- (c) 2 and 4 only
- (d) 3 and 4 only

26. For common-collector amplifier, the current gain ( $A_I$ ) is

- (a)  $1 + h_{fe}$
- (b)  $\frac{1 + h_{fe}}{1 + h_{oe}R_L}$
- (c)  $\frac{1 + h_{fe}}{h_{oe}h_{ie}}$
- (d)  $\frac{1 + h_{fe}}{1 + h_{ie}R_L}$

27. Consider the following statements :

1. Speed of operation of MOSFET is more than the speed of operation of SCR.
2. SCRs have lower power loss than MOSFETs.
3. The current in conducting state can easily be controlled through the gate in SCR.
4. MOSFET is not a current-triggered device.

The correct statements are

- (a) 1 and 4 only
- (b) 1 and 2 only
- (c) 2 and 3 only
- (d) 1, 2, 3 and 4

28. Match List-I with List-II and select the correct answer using the code given below the Lists :

<i>List-I</i>	<i>List-II</i>
A. $di/dt$ rating limits	1. Snubber circuit
B. $dv/dt$ rating limits	2. Heat sink
C. $i^2t$ limit	3. Series reactor
D. Junction temperature limit	4. Fuse

Code :

- (a) A B C D  
2 4 1 3
- (b) A B C D  
3 4 1 2
- (c) A B C D  
2 1 4 3
- (d) A B C D  
3 1 4 2

29. An SCR can be turned off

- (a) by passing a negative pulse to its gate
- (b) by removing the gate supply
- (c) by reverse biasing it
- (d) by forcing the current through gate to become zero

30. Body effect in MOSFETs results in

- (a) increase in the value of transconductance
- (b) change in the value of threshold voltage
- (c) decrease in the value of transconductance
- (d) increase in the value of output resistance

31. The efficiency of an LED for generating light is directly proportional to the

- (a) applied voltage
- (b) current injected
- (c) temperature
- (d) level of doping

32. A signal  $f(t)$  is described as

$$f(t) = [1 - |t|] \quad \text{when } |t| \leq 1$$

$$= 0 \quad \text{when } |t| > 1$$

This represents the unit

- (a) sinc function
- (b) area triangular function
- (c) signum function
- (d) parabolic function

33. Match List-I with List-II and select the correct answer using the code given below the Lists :

List-I

List-II

- |                    |   |
|--------------------|---|
| A. Even signal     | 1. $x(n) = \left(\frac{1}{4}\right)^n u(n)$ |
| B. Causal signal   | 2. $x(-n) = x(n)$                           |
| C. Periodic signal | 3. $x(t)u(t)$                               |
| D. Energy signal   | 4. $x(n) = x(n + N)$                        |

Code :

- |     |   |   |   |   |
|-----|---|---|---|---|
| (a) | A | B | C | D |
|     | 2 | 3 | 4 | 1 |
| (b) | A | B | C | D |
|     | 1 | 3 | 4 | 2 |
| (c) | A | B | C | D |
|     | 2 | 4 | 3 | 1 |
| (d) | A | B | C | D |
|     | 1 | 4 | 3 | 2 |

34. The period of the signal

$$x(t) = 10\sin 12\pi t + 4\cos 18\pi t$$

is

- (a)  $\frac{\pi}{4}$
- (b)  $\frac{1}{6}$
- (c)  $\frac{1}{9}$
- (d)  $\frac{1}{3}$

35. A linear time-invariant system has an impulse response of  $e^{2t}$ ,  $t > 0$ . If the initial conditions are zero and the input is  $e^{3t}$ , the output for  $t > 0$  is

- (a)  $e^{3t} - e^{2t}$
- (b)  $e^{5t}$
- (c)  $e^{3t} + e^{2t}$
- (d)  $e^t$

36. A system described by the following differential equation is initially at rest and then excited by the input  $x(t) = 3u(t)$  :

$$\frac{d^2 y}{dt^2} + 4 \frac{dy}{dt} + 3y = x(t)$$

The output  $y(t)$  is

- (a)  $1 - 1.5e^{-t} + 0.5e^{-3t}$
- (b)  $1 - 0.5e^{-t} + 1.5e^{-3t}$
- (c)  $1 + 1.5e^{-t} - 0.5e^{-3t}$
- (d)  $1 + 0.5e^{-t} - 0.5e^{-3t}$



37. The natural response of an LTI system described by the difference equation

$$y(n) - 1.5y(n-1) + 0.5y(n-2) = x(n)$$

is

(a)  $y(n) = 0.5u(n) - 2(0.5)^n u(n)$

(b)  $y(n) = 0.5u(n) - (0.5)^n u(n)$

(c)  $y(n) = 2u(n) - 0.5(0.5)^n u(n)$

(d)  $y(n) = 2u(n) - (0.5)^n u(n)$

38. Consider a system described by the state model

$$\dot{X} = \begin{bmatrix} 2 & 1 \\ -1 & 2 \end{bmatrix} X + \begin{bmatrix} 1 \\ 1 \end{bmatrix} U$$

$$Y = [1 \ 1] X$$

The system is

(a) controllable but not observable

(b) uncontrollable and observable

(c) both controllable and observable

(d) neither controllable nor observable

39. The system represented by the state-variable model

$$\dot{X} = \begin{bmatrix} 0 & -1 \\ 1 & -2 \end{bmatrix} X + \begin{bmatrix} 1 \\ 2 \end{bmatrix} U$$

is

(a) oscillatory

(b) critically damped

(c) over-damped

(d) under-damped

40. A second-order system represented by state variables has

$$A = \begin{bmatrix} -2 & -4 \\ 1 & 0 \end{bmatrix}$$

The values of natural frequency and damping factor are respectively

(a) 2 and 0.5

(b) 2 and 1

(c) 1 and 2

(d) 0.5 and 2

41. A waveform is given by  $v(t) = 10\sin 2\pi 100t$ . What will be the magnitude of the second harmonic in its Fourier series representation?

- (a) 0 V
- (b) 20 V
- (c) 100 V
- (d) 200 V

42. The property of Fourier transforms which states that the compression in time domain is equivalent to expansion in the frequency domain is

- (a) duality
- (b) scaling
- (c) time scaling
- (d) frequency shifting

43. The function which has its Fourier transform, Laplace transform and Z-transform unity is

- (a) Gaussian
- (b) impulse
- (c) sinc
- (d) pulse

44. The Fourier transform of a rectangular pulse is

- (a) another rectangular pulse
- (b) triangular pulse
- (c) sinc function
- (d) impulse function

45. Consider a system with transfer function

$$H(s) = \frac{3s^2 - 2}{s^2 + 3s + 2}$$

The step response of the system is given by

- (a)  $C(t) = 5e^{-2t} - e^{-t} - 1$
- (b)  $C(t) = 3\delta(t) - 10e^{-2t} + e^{-t}$
- (c)  $C(t) = 4e^{-t} - e^{-2t} - 1$
- (d)  $C(t) = 2(1 - e^{-2t})$

46. If  $F(s)$  and  $G(s)$  are the Laplace transforms of  $f(t)$  and  $g(t)$ , then their product  $F(s) \cdot G(s) = H(s)$ , where  $H(s)$  is the Laplace transform of  $h(t)$ , is defined as

- (a)  $(f \cdot g)(t)$
- (b)  $\int_0^t f(\tau) g(t - \tau) d\tau$
- (c) Both (a) and (b) are correct
- (d)  $f(t) \cdot g(t)$

47. With the following equations, the time-invariant systems are

1.  $\frac{d^2 y(t)}{dt^2} + 2t \frac{d}{dt} y(t) + 5y(t) = x(t)$

2.  $y(t) = e^{-2x(t)}$

3.  $y(t) = \left[ \frac{d}{dt} x(t) \right]^2$

4.  $y(t) = \frac{d}{dt} [e^{-2t} x(t)]$

(a) 1 and 2

(b) 1 and 4

(c) 2 and 3

(d) 3 and 4

48.  $H(e^{j\omega})$  is the frequency response of a discrete time LTI system and  $H_1(e^{j\omega})$  is the frequency response of its inverse function. Then

(a)  $H(e^{j\omega})H_1(e^{j\omega}) = 1$

(b)  $H(e^{j\omega})H_1(e^{j\omega}) = \delta(\omega)$

(c)  $H(e^{j\omega}) * H_1(e^{j\omega}) = 1$

(d)  $H(e^{j\omega}) * H_1(e^{j\omega}) = \delta(\omega)$

49. The impulse response of a discrete time system is given by

$$h(n) = \frac{1}{2}(\delta[n] + \delta[n-2])$$

The magnitude of the response can be expressed as

(a)  $|\cos \Omega|$

(b)  $\cos \Omega$

(c)  $|\sin \Omega|$

(d)  $\sin \Omega$

50. The discrete time system described by  $y(n) = x(n)^2$  is

(a) causal and linear

(b) causal and non-linear

(c) non-causal and linear

(d) non-causal and non-linear

51. The difference equation for a system is given by

$$y(n+2) + y(n+1) + 0.16y(n) = x(n+1) + 0.32x(n)$$

The transfer function of the system is

(a)  $\frac{Z + 0.32}{Z^2 + Z + 0.16}$

(b)  $\frac{1}{Z^2 + Z + 0.16}$

(c)  $\frac{Z + 0.32}{Z^2 + 0.16}$

(d)  $\frac{Z + 0.32}{(Z-1)(Z^2 + Z + 0.16)}$

52. The Z-transform corresponding to the Laplace transform function

$$G(s) = \frac{10}{s(s+5)}$$

is

(a)  $\frac{2Ze^{-5Z}}{(Z-1)(Z-e^{-T})}$

(b)  $\frac{2(1-e^{-5T})Z}{(Z-1)(Z-e^{-5T})}$

(c)  $\frac{e^{-5T}}{(Z-1)^2}$

(d)  $\frac{e^{-T}}{Z(Z-e^{-3T})}$

53. The step response of a discrete time system with transfer function

$$H(Z) = \frac{10}{(Z-1)(Z+2)}$$

is given by

(a)  $\frac{-10}{9} + \frac{10}{3}n + \frac{10}{9}(-2)^n$

(b)  $-5 + \frac{n}{2} + (-2)^n$

(c)  $\frac{-7}{9} + \frac{5}{3}n + (-3)^n$

(d)  $-2 + 5(1-2^n)$

54. The probability cumulative distribution function must be monotone and

(a) increasing

(b) decreasing

(c) non-increasing

(d) non-decreasing

55. A random variable is known to have a cumulative distribution function

$$F_X(x) = U(x) \left( 1 - \frac{x^2}{b} \right)$$

Its density function is


(a)  $U(x) \frac{2x}{b} (1 - e^{-x^2/b})$

(b)  $U(x) \frac{2x}{b} e^{-x^2/b}$

(c)  $U(x) \left( 1 - \frac{x^2}{b} \right) \delta(x)$

(d)  $\left( 1 - \frac{x^2}{b} \right) \delta(x) + e^{-x^2/b}$

56.

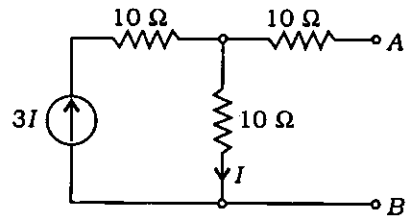

In the circuit shown, Thevenin's voltage as seen from the terminals AB is


(a) 0 V

(b) 1.5 V

(c) 6.0 V

(d) indeterminate


57.

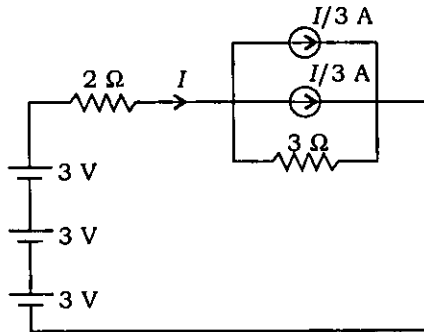

In the circuit, the voltage across  $3\ \Omega$  resistance is

- (a) 1 V
- (b) 3 V
- (c) 6 V
- (d) 9 V


58.

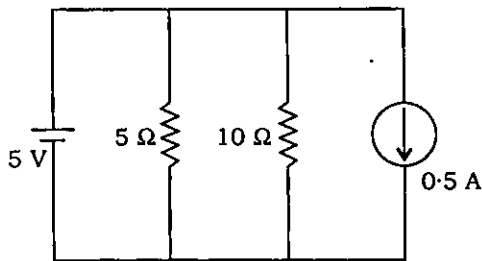

The total resistance faced by the voltage source having zero internal resistance in the circuit is

- (a)  $10\ \Omega$
- (b)  $5\ \Omega$
- (c)  $2.5\ \Omega$
- (d)  $1.5\ \Omega$


59.

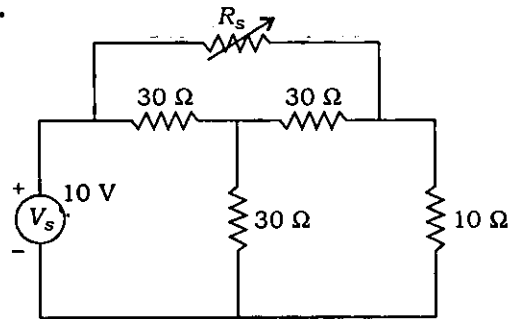

In the circuit, the value of the resistance  $R_s$  required for maximum power transfer from the 10 V source to the  $10\ \Omega$  load is given by

- (a)  $5\ \Omega$
- (b)  $10\ \Omega$
- (c)  $0\ \Omega$
- (d)  $30\ \Omega$


60.

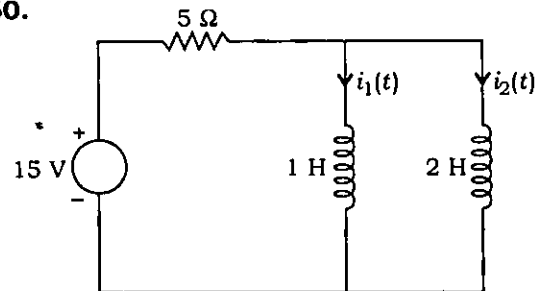

The steady-state values of the currents  $i_1(t)$  and  $i_2(t)$  in the circuit are

- (a) 2 A and 1 A
- (b) 1.5 A and 1.5 A
- (c) 1 A and 2 A
- (d) 1 A and 1 A


61.

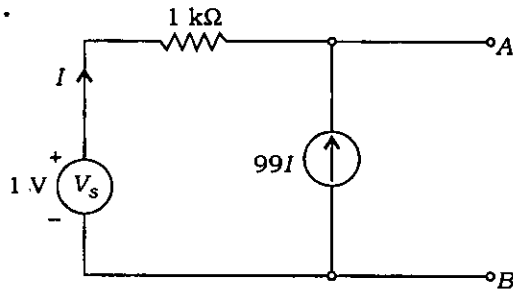

Thevenin's equivalent resistance as seen from the terminals  $AB$  for the circuit is

- (a)  $1 \text{ k}\Omega$
- (b)  $10 \text{ }\Omega$
- (c)  $100 \text{ }\Omega$
- (d)  $10 \text{ k}\Omega$


62.

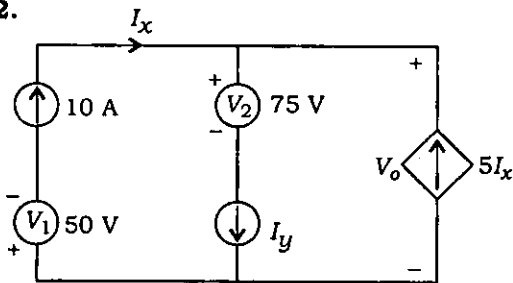

The total power developed in the circuit, if  $V_o = 125 \text{ V}$  is

- (a) 0 watt
- (b) 4000 watts
- (c) 8000 watts
- (d) 16000 watts


63.

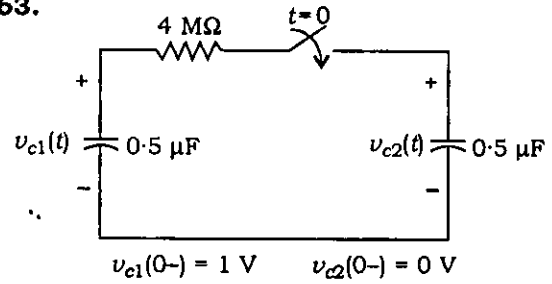

In the circuit given, the switch is closed at  $t = 0+$ . The initial voltages on the capacitors are indicated in the diagram. The voltages  $v_{c1}(t)$  and  $v_{c2}(t)$  for  $t \geq 0$  are respectively

- (a)  $\frac{1}{2}(1 - e^{-t})$  and  $\frac{1}{2}(1 + e^{-t})$
- (b)  $(1 - e^{-t})$  and  $(1 + e^{-t})$
- (c)  $\frac{1}{2}(1 + e^{-t})$  and  $\frac{1}{2}(1 - e^{-t})$
- (d)  $\frac{1}{2}(1 + e^{-t})$  and  $(1 - e^{-t/2})$

64.

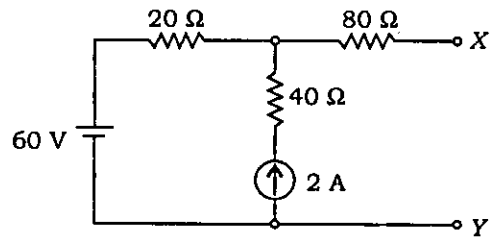

In the circuit, Thevenin's voltage and resistance across the terminals  $XY$  will be

- (a) 20 V and  $100 \text{ }\Omega$
- (b) 40 V and  $93.33 \text{ }\Omega$
- (c) 60 V and  $93.33 \text{ }\Omega$
- (d) 100 V and  $100 \text{ }\Omega$

65. A voltage of 24 V DC is applied through switch  $S$  to an  $R$ - $L$  series circuit. Switch  $S$  was initially open. At time  $t = 0$ , switch is closed. The rate of change of current through the resistor is 8 A/s, while the current through the inductor is 8 A. If the value of the inductor is 1 H, then for this condition the value of the resistor will be

- (a) 1  $\Omega$
- (b) 2  $\Omega$
- (c) 3  $\Omega$
- (d) 4  $\Omega$

66. The steady-state response of a network to the excitation  $V\cos(\omega t + \phi)$  may be found in three steps. The first two steps are as follows :

1. Determining the response of the network to the excitation  $e^{j\omega t}$
2. Multiplying the above response by  $\bar{V} = Ve^{-j\phi}$

The third step is

- (a) finding the complex conjugate of the expression after step 2
- (b) finding the magnitude of the expression after step 2
- (c) finding the real part of the expression after step 2
- (d) finding the imaginary part of the expression after step 2

67. The unit step response  $y(t)$  of a linear system is

$$y(t) = (1 - 3e^{-t} + 3e^{-2t})u(t)$$

For the system function, the frequency at which the forced response becomes zero is

- (a)  $\frac{1}{\sqrt{2}}$  rad/s
- (b)  $\frac{1}{2}$  rad/s
- (c)  $\sqrt{2}$  rad/s
- (d) 2 rad/s

68. For a given connected network and for a fixed tree, the fundamental loop matrix is given by

$$B = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & -1 \\ 0 & 0 & 1 & 1 & -1 & -1 \end{bmatrix}$$

The fundamental cut-set matrix  $Q$  corresponding to the same tree is given by

$$(a) \quad Q = \begin{bmatrix} -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 1 & 0 \\ 0 & 1 & 1 & 0 & 0 & 1 \end{bmatrix}$$

$$(b) \quad Q = \begin{bmatrix} -1 & 0 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 0 & 1 & 0 \\ 0 & 1 & 1 & 0 & 0 & 1 \end{bmatrix}$$

$$(c) \quad Q = \begin{bmatrix} 1 & 0 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 0 & 1 & 0 \\ 0 & 1 & 1 & 0 & 0 & 1 \end{bmatrix}$$

$$(d) \quad Q = \begin{bmatrix} 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & -1 \\ 1 & 0 & 1 & 1 & -1 & -1 \end{bmatrix}$$

69. For a two-port network,  $V_1$  and  $V_2$  are given by

$$V_1 = 60I_1 + 20I_2$$

$$V_2 = 20I_1 + 40I_2$$

The Y-parameters of the network are

(a)  $Y_{11} = 20 \times 10^{-3}$   
 $Y_{12} = -10 \times 10^{-3}$   
 $Y_{21} = -10 \times 10^{-3}$   
 $Y_{22} = 30 \times 10^{-3}$

(b)  $Y_{11} = -10 \times 10^{-3}$   
 $Y_{12} = 20 \times 10^{-3}$   
 $Y_{21} = 20 \times 10^{-3}$   
 $Y_{22} = -30 \times 10^{-3}$


(c)  $Y_{11} = 10 \times 10^{-3}$   
 $Y_{12} = -20 \times 10^{-3}$   
 $Y_{21} = -20 \times 10^{-3}$   
 $Y_{22} = 30 \times 10^{-3}$

(d)  $Y_{11} = -20 \times 10^{-3}$   
 $Y_{12} = 10 \times 10^{-3}$   
 $Y_{21} = 10 \times 10^{-3}$   
 $Y_{22} = -30 \times 10^{-3}$

70. The  $h_{11}$  and  $h_{22}$  of a standard T-network with series impedances  $2 \Omega$  and  $7 \Omega$ , and shunt branch impedance of  $3 \Omega$  are

- (a)  $5 \Omega$  and  $10 \text{ mho}$  respectively  
 (b)  $10 \Omega$  and  $5 \text{ mho}$  respectively  
 (c)  $5 \Omega$  and  $0.1 \text{ mho}$  respectively  
 (d)  $10 \Omega$  and  $0.2 \text{ mho}$  respectively

71.

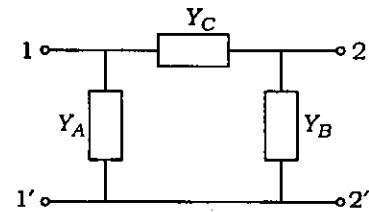

For the two-port network shown, the parameter  $Y_{12}$  is equal to

- (a)  $Y_C$   
 (b)  $Y_C + Y_B$   
 (c)  $Y_A + Y_C$   
 (d)  $-Y_C$

72. The transmission parameter matrix  $[T]$  for an ideal transformer with a turns ratio of  $n_1 : n_2$  is given by

(a) 
$$\begin{bmatrix} \frac{n_1}{n_2} & 1 \\ 0 & \frac{n_2}{n_1} \end{bmatrix}$$

(b) 
$$\begin{bmatrix} \frac{n_1}{n_2} & 0 \\ 0 & \frac{n_2}{n_1} \end{bmatrix}$$

(c) 
$$\begin{bmatrix} \frac{n_1}{n_2} & 1 \\ 0 & -\frac{n_2}{n_1} \end{bmatrix}$$

(d) 
$$\begin{bmatrix} \frac{n_1}{n_2} & 0 \\ 1 & -\frac{n_2}{n_1} \end{bmatrix}$$



73. A two-port network has parameters  $ABCD$ . If all the impedances in the network are doubled, then

(a)  $A$  and  $D$  remain unchanged,  $B$  is doubled and  $C$  is halved

(b)  $A$ ,  $B$ ,  $C$  and  $D$  are all doubled

(c)  $A$  and  $D$  are doubled,  $C$  and  $B$  remain unchanged

(d)  $A$  and  $D$  remain unchanged,  $C$  is doubled and  $B$  is halved

74. The conditions under which a passive two-port network represented by  $ABCD$  is reciprocal and symmetrical are

(a)  $AD - BC = 1$ ;  $A = C$

(b)  $AD - BC = 0$ ;  $A = D$

(c)  $AD - BC = 1$ ;  $D = A$

(d)  $AD - BC = 0$ ;  $C = B$

75. The maximum power that a 12 V DC source with an internal resistance of  $2 \Omega$  can supply to a resistive load is

(a) 72 W

(b) 48 W

(c) 24 W

(d) 18 W

76. A two-terminal network consists of a coil having inductance  $L$  and resistance  $R$  shunted by a capacitance  $C$ . The poles and zeros of the driving-point impedance function  $Z(\omega)$  are located as poles at  $-\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$  and zero at  $-1$ . If  $Z(0) = 1$ , the values of  $R$ ,  $L$  and  $C$  are


(a)  $1 \Omega$ ,  $1 \text{ H}$  and  $1 \mu\text{F}$

(b)  $1 \Omega$ ,  $1 \text{ H}$  and  $1 \text{ F}$

(c)  $1 \Omega$ ,  $1 \mu\text{H}$  and  $1 \text{ F}$

(d)  $1 \text{ k}\Omega$ ,  $1 \text{ H}$  and  $1 \text{ F}$

77.

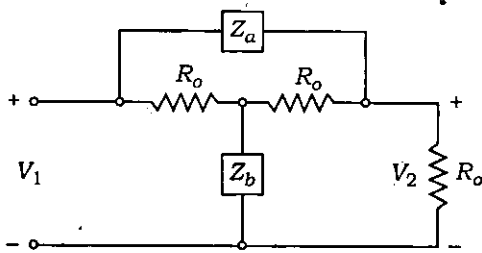

The condition under which the input impedance at port 1 for the above network will be equal to  $R_o$  is

(a)  $Z_a + Z_b = R_o$

(b)  $Z_a Z_b = R_o^2$

(c)  $Z_a / Z_b = 1$

(d)  $Z_b / Z_a = 1/2$

78. If the potential difference between points  $A(1, 0, 0)$  and  $B(2, 0, 0)$  is 10 V, determine  $d$  for point  $C(d, 0, 0)$ , when  $V_{BC}$  is 6 V in a uniform field.

(a) 1 m

(b) 2 m

(c) 6 m

(d) 5 m

79. There are three charges, which are given by  $Q_1 = 1 \mu\text{C}$ ,  $Q_2 = 2 \mu\text{C}$  and  $Q_3 = 3 \mu\text{C}$ . The field due to each charge at a point  $P$  in free space is  $(a_x + 2a_y - a_z)$ ,  $(a_y + 3a_z)$  and  $(2a_x - a_y)$  newtons/coulomb. The total field at the point  $P$  due to all three charges is given by

(a)  $1 \cdot 6a_x + 2 \cdot 2a_y + 2 \cdot 5a_z$   
newtons/coulomb

(b)  $0 \cdot 3a_x + 0 \cdot 2a_y + 0 \cdot 2a_z$   
newtons/coulomb

(c)  $3a_x + 2a_y + 2a_z$   
newtons/coulomb

(d)  $0 \cdot 6a_x + 0 \cdot 2a_y + 0 \cdot 5a_z$   
newtons/coulomb

80. The credit of defining the following current is due to Maxwell

(a) Conduction current

(b) Drift current

(c) Displacement current

(d) Diffusion current

81. For a plane wave propagating in an unbounded medium (say, free space), the minimum angle between electric field and magnetic field vectors is

- (a)  $0^\circ$
- (b)  $60^\circ$
- (c)  $90^\circ$
- (d)  $180^\circ$

82. A  $75 \Omega$  transmission line is first short-terminated and the minima locations are noted. When the short is replaced by a resistive load  $R_L$ , the minima locations are not altered and the VSWR is measured to be 3. The value of  $R_L$  is

- (a)  $25 \Omega$
- (b)  $50 \Omega$
- (c)  $225 \Omega$
- (d)  $250 \Omega$

83. A  $\lambda/4$  line, shorted at one end, presents impedance at the other end equal to

- (a)  $Z_0$
- (b)  $\sqrt{2}Z_0$
- (c)  $\infty$
- (d)  $0$

where  $Z_0$  is characteristic impedance of the line.

84. A plane wave travelling in a medium of  $\epsilon_r = 1$ ,  $\mu_r = 1$  (free space) has an electric field intensity of  $100\sqrt{\pi}$  V/m. Determine the total energy density of this magnetic field.

- (a)  $13.9 \text{ nJ/m}^3$
- (b)  $27.8 \text{ nJ/m}^3$
- (c)  $139 \text{ nJ/m}^3$
- (d)  $278 \text{ nJ/m}^3$

85. With the symbols having their standard meanings, cut-off frequency (frequency below which wave propagation will not occur) for a rectangular waveguide is

$$(a) \frac{1}{\sqrt{\mu\epsilon}} \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2}$$

$$(b) \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2}$$

$$(c) \frac{1}{2\pi\sqrt{\mu\epsilon}} \left(\frac{m\pi}{a}\right) + \left(\frac{n\pi}{b}\right)$$

$$(d) \frac{1}{\sqrt{\mu\epsilon}} \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2}$$

86.

$$n = \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2 - \omega^2\mu\epsilon}$$

represents the propagation constant in a rectangular waveguide for

(a) TE waves only

(b) TM waves only

(c) TEM waves

(d) TE and TM waves

87. Consider a rectangular waveguide of internal dimensions 8 cm × 4 cm. Assuming an  $H_{10}$  mode of propagation, the critical wavelength would be

(a) 8 cm

(b) 16 cm

(c) 4 cm

(d) 32 cm

88. The ratio of the transverse electric field to the transverse magnetic field is called as

(a) waveguide impedance.

(b) waveguide wavelength

(c) phase velocity

(d) Poynting vector

89. The directivity of a  $\lambda/2$  long wire antenna is

(a) 1.5

(b) 1.66

(c) 2

(d)  $\sqrt{2}$ 

90. During measurement of voltage and current in a load, ammeter and voltmeter are connected in series and across the load respectively. If ammeter and voltmeter positions are interchanged by mistake, then

(a) voltmeter will be damaged

(b) ammeter will be damaged

(c) both the meters will be damaged

(d) both the meters will be safe

91. A resistance is measured by a voltmeter-ammeter method using DC excitation and a voltmeter of very high resistance connected directly across the unknown resistance. If the voltmeter and ammeter are subject to maximum error of  $\pm 2.4\%$  and  $\pm 1.0\%$  respectively, then the magnitude of maximum error in the value of resistance obtained from the measurement is nearly

(a) 1.4%

(b) 1.7%

(c) 2.4%

(d) 3.4%

92. For the recording of very fast random signals, the most suitable instrument would be
- (a) dual-trace
  - (b) sampling oscilloscope
  - (c) real-time spectrum analyzer
  - (d) scanning-type spectrum analyzer
93. To increase the range of a voltmeter
- (a) a low resistance in series is connected with the voltmeter
  - (b) a low resistance in parallel is connected with the voltmeter
  - (c) a high resistance in series is connected with the voltmeter
  - (d) a high resistance in parallel is connected with the voltmeter
94. The following type of instrument can be used for measuring AC voltage of the highest frequency with reasonable accuracy
- (a) Electrodynamometer
  - (b) Moving-iron
  - (c) Thermal-thermoelectric
  - (d) Rectifier
95. The null balance potentiometric measurement of voltage technique is **not** capable of measuring
- (a) DC voltage
  - (b) AC voltage
  - (c) voltage with higher accuracy and sensitivity as compared to deflection-type instrument
  - (d) dynamic and transient voltage changes
96. A d'Arsonval meter of 100  $\Omega$  DC coil and 0-1 mA sensitivity gives full-scale reading of 10 A on using an external resistance of
- (a) 100  $\Omega$
  - (b) 10  $\Omega$
  - (c) 0.01  $\Omega$
  - (d) 0.001  $\Omega$
97. Lissajous pattern shown in a double-beam cathode-ray oscilloscope screen for two sinusoidal voltages of equal magnitude and of the same frequency but of phase shift of 30° electrical is
- (a) a circle
  - (b) a straight line at 45° in the first and third quadrant
  - (c) an ellipse in the first and third quadrant
  - (d) an ellipse in the second and fourth quadrant

98. A Q-meter is supplied with an oscillator having a 500 mV output voltage. While testing an unknown inductor, the voltage across the variable capacitor of the Q-meter, measured by a digital voltmeter, is obtained as 10 V. The Q-factor of the inductor is

- (a) 5
- (b) 10
- (c) 20
- (d) 0.05

99. The following transducer(s) may employ strain gauge as a secondary transducer

- (a) Load cell only
- (b) Load cell and torquemeter only
- (c) Load cell, torquemeter and accelerometer only
- (d) Load cell, torquemeter, accelerometer and flowmeter

100. In a digital frequency meter, the Schmitt trigger is used for

- (a) converting sinusoidal waveforms into rectangular pulses
- (b) scaling of sinusoidal waveforms
- (c) providing timebase
- (d) triggering a start pulse

101. Moving-coil permanent magnet instruments can be used for the measurement of

- (a) AC and DC
- (b) AC only
- (c) DC only
- (d) half-wave rectified DC

102. For controlling the vibration of the disc of an AC energy meter, damping torque is produced by

- (a) eddy current
- (b) chemical effect
- (c) electrostatic effect
- (d) magnetic effect

103. Analog inputs are converted to digital outputs using op-amps as comparators. Assuming a 5-bit digital output, the number of comparators required would be

- (a) 32
- (b) 31
- (c) 64
- (d) 63

104. The value of  $n$  for the  $n$ -bit A/D converter required to convert an analog input in the range of 0 to 5 volts to an accuracy of 10 mV is
- (a) 8
  - (b) 9
  - (c) 7
  - (d) 6
105. One of the following can act as an inverse transducer
- (a) Electrical resistance potentiometer
  - (b) LVDT
  - (c) Piezoelectric crystal
  - (d) Capacitive transducer
106. Two strain gauges are used to measure strain in a cantilever, one gauge is mounted on the top of the cantilever and the other is placed at the bottom. The two strain gauges form two arms of Wheatstone's bridge. This bridge configuration is called
- (a) a quarter bridge
  - (b) a half bridge
  - (c) a full bridge
  - (d) a null bridge
107. A Hall effect transducer is generally used for the measurement of
- (a) power
  - (b) current
  - (c) displacement
  - (d) voltage
108. A digital linear displacement transducer normally uses
- (a) straight binary code
  - (b) binary coded decimal
  - (c) Gray code
  - (d) hexadecimal code.
109. The following transducer is used for accurate and precise measurement of temperature
- (a) Thermistor
  - (b) Thermocouple  
(Alumel / Chromel)
  - (c) Semiconductor temperature sensor chip
  - (d) Platinum resistance thermometer
110. Electrical voltage-based telemetering schemes used for short distances must necessarily have
- (a) low current level only
  - (b) small signal power only
  - (c) high signal to noise ratio  $\left(\frac{S}{N} \gg 2\right)$  only
  - (d) All of the above

111. Electrical positional system telemetering uses for transmission of signal in

- (a) two wires only
- (b) two or three wires only
- (c) two or three or four wires only
- (d) two or three or four or even five wires

*Directions :*

Each of the following **nine (9)** items consists of two statements, one labelled as 'Statement (I)' and the other as 'Statement (II)'. You are to examine these two statements carefully and select the answers to these items using the code given below :

*Code :*

- (a) Both Statement (I) and Statement (II) are individually true and Statement (II) is the correct explanation of Statement (I)
- (b) Both Statement (I) and Statement (II) are individually true but Statement (II) is **not** the correct explanation of Statement (I)
- (c) Statement (I) is true but Statement (II) is false
- (d) Statement (I) is false but Statement (II) is true

112. Statement (I) :

All substances except ferromagnetic materials which can form permanent magnets, exhibit magnetic effects.

Statement (II) :

Their magnetic effect is due to alignment of dipoles when subjected to an external electromagnetic field.

113. Statement (I) :

Concentration of acceptor atoms in the region between isolation islands in a monolithic integrated circuit will be much higher than in the  $p$ -type substrate.

Statement (II) :

The higher density is provided to prevent the depletion region of the reverse-biased isolation to substrate junction from extending into the  $p^+$ -type material.

114. Statement (I) :

The gate of MOSFET is insulated from the body of FET by deposition of a very thin fragile layer of  $\text{SiO}_2$  over the substrate.

Statement (II) :

The device is therefore called as an insulated gate field-effect transistor (IGFET).



115. Statement (I) :

Z-transform approach is used to analyze the discrete time systems and is also called as pulse transfer function approach.

Statement (II) :

The sampled signal is assumed to be a train of impulses whose strengths, or areas, are equal to the continuous time signal at the sampling instants.

116. Statement (I) :

Lossless network functions have only imaginary zeros and poles with only negative real parts.

Statement (II) :

Lossless network functions obey the separation property.

117. Statement (I) :

Resistance hygrometer is a good humidity transducer.

Statement (II) :

Resistance hygrometer has a sensing element and absorbs or gives up moisture till equilibrium is reached with ambient water-vapour pressure.

118. Statement (I) :

Dual-slope A/D converter is the most preferred A/D conversion approach in digital multimeters.

Statement (II) :

Dual-slope A/D converter provides high accuracy in A/D conversion, while at the same time suppressing the hum effect on the input signal.

119. Statement (I) :

RF voltage is measured by rectifying the alternating voltage first and then amplifying the resulting DC output.

Statement (II) :

Amplification of RF signals is itself a very difficult task.

120. Statement (I) :

Digital universal counter timer is used to measure time period and frequency of various circuits which are assembled together to form one complete block.

Statement (II) :

Digital counters use logic gates which are selected and controlled by a single front panel switch known as function switch which can be in either frequency or time-base mode.

**SPACE FOR ROUGH WORK**

**SPACE FOR ROUGH WORK**

SPACE FOR ROUGH WORK

\*\*\*

R-FTF-M-FUA/54A

28

SJ-76\*300